

**SEMICONDUCTOR KIT FOR  
POWER FACTOR CORRECTOR**

by J. M. Borgeous

*This paper present a new line of P.F.C. dedicated products. Both silicon and packaging have been optimized to reduce system cost, including filtering. The products shown here are offered as a kit for power factor correction.*


**BOOST CIRCUIT OPTIMIZATION PARAMETERS**

Among the available topologies, a boost circuit operating in continuous current mode is the only topology which enables the RFI noise across the input capacitor to be limited, and consequently a lower cost filter is required. Also, the boost inductor stores only a part of the transferred energy, because the mains still supplies energy during the demagnetization phase of the boost inductor - so the magnetic part required is smaller than needed with any other topology. Therefore the boost topology leads to the cheapest solution.

Figure 1 shows the general topology of a boost PFC. Its optimization requires careful adjustment of the following parameters:

- the value of the input capacitor  $C_i$
- the current ripple in the boost inductor  $L_b$
- the parasitic capacitances of the boost inductor and power semiconductors, including those associated with the heatsink
- the operating frequency and also the frequency modulation technique.

**Figure 1:** Semiconductor Kit for PFC Schematic.

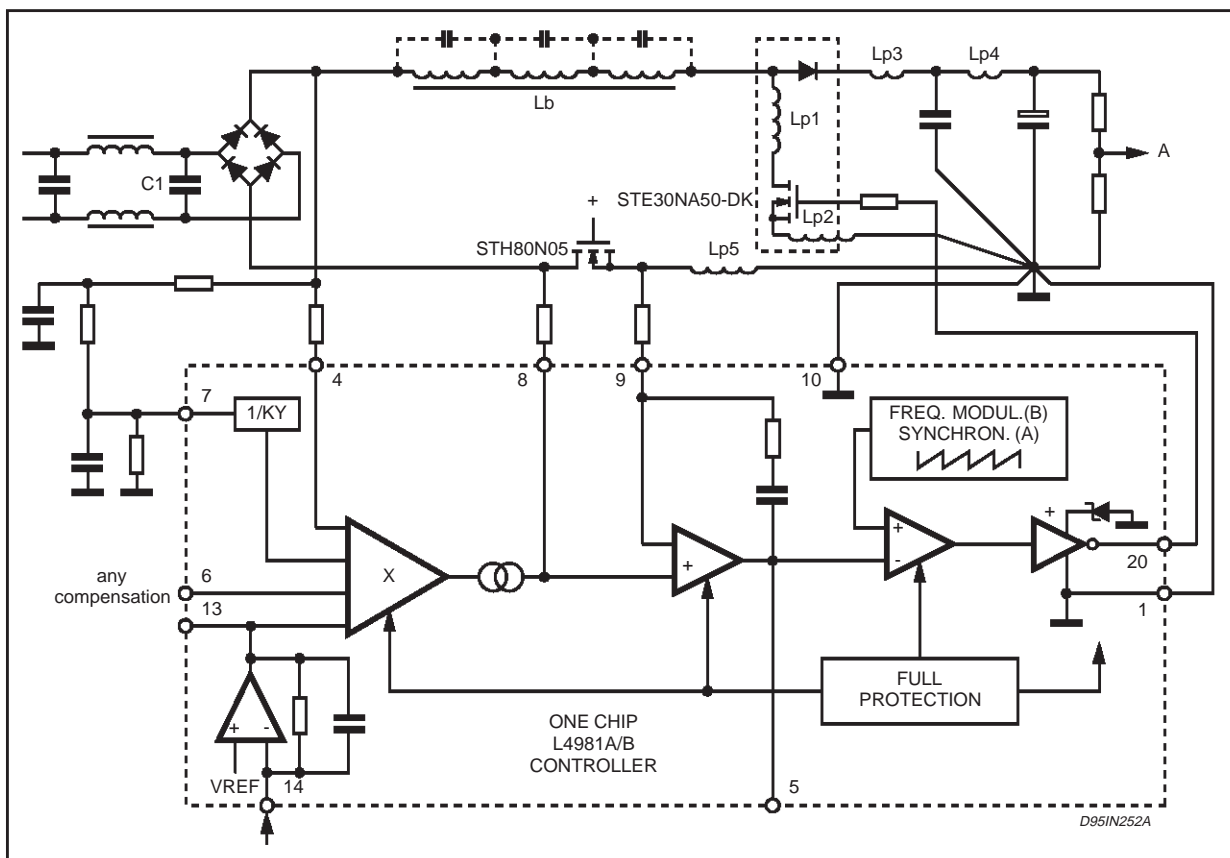

## APPLICATION NOTE

---

### SEMI-CONDUCTOR KIT

The semiconductor kit consists of an L4981 controller, an STE36N50-DK power module and an STH80N05 power sense (see figure 1).

#### L4981A/B controller:

The L4981 operates with an input voltage range of 85V to 270V and uses average current mode PWM control, providing feed forward line and load compensation. Two versions are available: version (A) provides synchronization with the down stream converter, whereas version (B) provides linear frequency modulation, spreading the RFI noise spectrum.

Both versions incorporate overvoltage and over-current protection, soft start and under voltage lockout with programmable threshold.

Other features include an on chip voltage reference (2%) which is externally available, a typical starting current of only 0.5mA and separate grounds for the power and signal stages.

L4981 use an optimum current control method. It is an average current control using feed forward line regulation and variable or fixed switching frequency. The oscillator simultaneously turns on the power switch and starts the ramp of the PWM current control. The average inductor current is compared with the current reference by means of the current error amplifier. It operates as an integrator, allowing the circuit to accurately follow the current reference generated by the multiplier. This current reference is obtained by sinewave modulating the error voltage of the voltage control loop. A feed forward compensation of the mains voltage has been added to the multiplier in order to keep constant the voltage control loop bandwidth whatever the mains fluctuation. A fourth multiplier input allows external compensation to be applied to the current modulation.

The oscillator can operate at constant or modulated switching frequency. In applications where modulated frequency is used, the RFI noise spectrum can be spread adjusting the depth of modulation by means of an external resistor. Then the maximum inductor current occurs at the minimum operating frequency.

#### STE30NA50-DK Power Module:

Built in an isolated ISOTOP™ package, which can be mounted directly on a PCB, this module integrates a low  $R_{DS(ON)}$  Power MOSFET and a TURBOSWITCH™ Diode. Putting these two components in a single isolated package with

very low parasitic inductance and capacitance reduces the component count, and significantly reduces transient overvoltages, and EMI and RFI.

As a result, the design safety margin can be relaxed and the voltage rating of the power MOSFET can be just  $500V_{(br)DSS}$ , meaning also that the  $R_{DS(on)}$  of the MOSFET can be lower - in this case it is 0.14 Ohm. Both the current and avalanche handling capabilities of the power MOSFET section are specified at 100°C junction temperature, allowing for maximum utilization of the device. The MOSFET is a low gate-charge type and so its drive requirements are compatible with the 2A peak current capability of the L4981 controller.

The integrated TURBOSWITCH™ freewheeling diode is an ultra-fast, soft recovery device using planar epitaxial technology, and is a part of the STTA series. Its low  $t_{rr}$  (30ns) keeps the MOSFET switching losses to a minimum. Other ratings are  $600V_{RRM}$  and a maximum  $V_F$  of 1.5V at the rated average forward current ( $I_{Fav} = 20A$ ).

#### STH80N05 Power sense:

Using a high density low voltage Power MOSFET for current sensing has many advantages:

- low resistance, typically 10m $\Omega$
- Can be mounted on the same heatsink as the ISOTOP
- intrinsic diode for controller input protection
- very low parasitic inductance improving signal/noise ratio.

However, the peak current limitation will be affected by the MOSFET thermal characteristic.

#### DESIGN RULE EXAMPLE

Taking the following operating conditions (see figure 2):

$$V_{in\ rms} = 230Vac +10\% -15\% \quad (f=50Hz)$$

$$I_{in\ rms} = 16Arms$$

$$P_{out} = 3000W$$

$$V_{out} = 400Vdc$$

or

$$V_{in\ rms} = 120Vac +20\% -20\% \quad (f=60Hz)$$

$$I_{in\ rms} = 15Arms$$

$$P_{out} = 1400W$$

$$V_{out} = 400Vdc$$




## APPLICATION NOTE

**SWITCHING FREQUENCY  $f_s$**  is kept below 50kHz to maintain the RFI noise within the optimum frequency range of the VFG 243 standard. Figure 3 shows that in the range of 10kHz/50kHz the switching frequency fundamental spectrum requires less filtering.

C18 = 2.2nF and R17 = 24k $\Omega$  give a switching frequency of 46kHz.

**Figure 3: VFG 243 LIMITS**

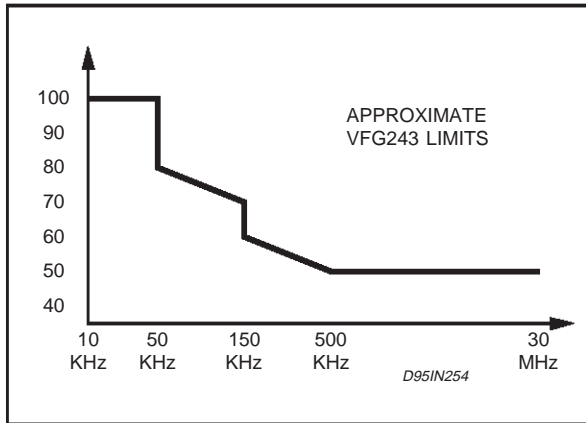

**BOOST INDUCTOR:** For applications in the range of 3kW, the boost inductor design is greatly determined by material choice and core availability.

As mentioned the inductor parasitic capacitance determines the filter requirements in the range 1MHz-30MHz (with regards to the switching noise). To keep this capacitance as low as possible, a single layer winding is the best solution, but this requires the use of a toroidal core shape to balance winding turns and core section. In this case a material with distributed air gaps, for example iron powder, is a good choice (see #2). This is the cheapest core material available with an inherently high saturation flux density combined with a distributed air gap.

Test have been performed using two different cores:

- T300-26D core from MICROMETAL (Anaheim, CA) made of iron powder / 60 turns / 12 AWG.
- 2 x CO55866A2 core from MAGNETICS, made of nickel, iron and molybdenum / 46 turns / 12 AWG.

**OUTPUT CAPACITANCE** value depends upon the expected output voltage drop during the specified holdup time. Considering a value of 2000F, the voltage drop during a 10msec holdup can be calculated from:

$$P_{out} \cdot 10\text{msec} = 1/2 C_{out} (V_{out} - V_{min})$$


then  $V_{min} = 382\text{V}$  at 1400W  
and  $V_{min} = 360\text{V}$  at 3000W

### FEED FORWARD COMPENSATION:

Pin 7 should be supplied with a voltage proportional to the rms mains voltage. This voltage must be in the range of 1.5V to 5.5V.

The circuit shown in figure 4 gives a good compromise between response time and harmonic attenuation with the following values: C71=68nF, C72 = 1 $\mu$ F, R71=820k $\Omega$ , R72 = 1 00k $\Omega$  and R73 = 22k $\Omega$ .

**Figure 4: Feed Forward Compensation Network**

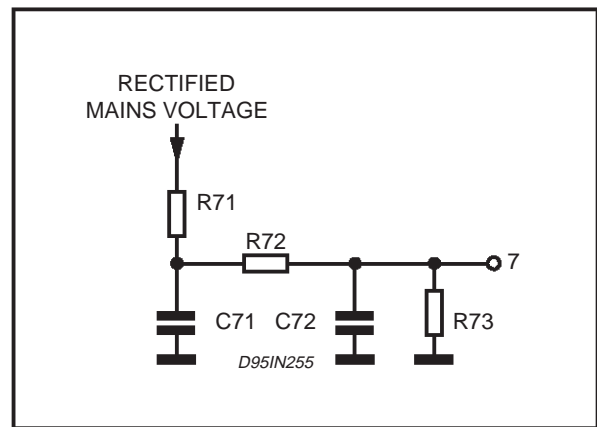

### VOLTAGE ERROR AMPLIFIER:

Operating with  $P_{out}=3000\text{W}$  and  $V_{out}=400\text{Vdc}$ , the mean  $I_{out}$  is 7.5A. The corresponding 100Hz capacitor current is defined by:

$$I_{capa} = (P_{out} / V_{out}) \cos 4!ft$$

So the peak current is:  $P_{out}/V_{out} = 7.5\text{A}$

Then the output voltage ripple  $V_r$  can be evaluated as:

$$V_r = 7.5\text{A} / 2\pi \cdot 100 \cdot 3500 \cdot E-6 = 6\text{Vpeak}$$

Voltage divider R141/R142 attenuates the output voltage ripple to:

$$V_{ri} = 6\text{Vpeak} \times 5.1/400 = 0.0765\text{Vpeak}$$

Assuming 3% peak voltage ripple at the voltage error amplifier output, ripple can be evaluated as:

$$V_{ro} = (5.1\text{V} - 1.27\text{V}) \cdot 0.03 = 0.115\text{Vpeak}$$

where the first term is the output error amplifier voltage range.

Then the global voltage error amplifier gain at 100Hz must be:

$$G_{vea} = V_{ro}/V_{ri} = 0.115/0.0765 = 1.5$$

as  $G_{vea} \# 1 / R14 \cdot 2\pi f \cdot C13$

with  $R_{14} = 47k\Omega$  then  $C_{13} = 22nF$

To maintain voltage loop stability requires the placement of a pole at a unity-gain frequency of about 18Hz (see #5)

then  $R_{13}C_{13} = 1/2\pi \cdot 18$

and  $R_{13} = 390k\Omega$

### LOAD COMPENSATION:

A voltage applied at pin 6 can be used to perform compensation, for example a load feed forward compensation. With reference to the multiplier section, this input is equivalent to the voltage error amplifier output. If not used, it should be connected to the reference voltage (pin 11).

**MULTIPLIER** circuit has the following response:

$I_{mult} = K_{mult} I_{ac} (V_{vea} - 1.27) (0.8LFF - 1.27) / V_{rms}$

where:

$K_{mult}$  is the multiplier constant (.37)

$V_{vea}$  is the voltage error amplifier output.

LFF is the voltage at pin 6.

$I_{ac}$  is the current supplied into pin 4.

$V_{rms}$  is voltage at pin 7.

To keep the maximum multiplier output current below  $300\mu A$ ,  $R_4$  should be set to  $1M\Omega$ , meaning  $I_{ac}$  rms varies from  $95\mu A$  to  $270\mu A$  rms.

The previous equation gives:  $I_{mult} \# 60\mu A$  rms with  $V_{in} = 95V_{rms}$  and  $P_{out} = 1400W$ , or  $V_{in} = 195V_{rms}$  and  $P_{out} = 3000W$ .

### CURRENT AMPLIFIER SECTION:

Using a low  $R_{DSon}$  Power MOSFET as current sense instead of a resistance leads to a reduction of the parasitic inductance and allows the heat generated to be dissipated in the heatsink. Using the specifications of the STH80N05,  $R_{sense}$  max is  $11m\Omega$  at  $25^\circ C$  and  $15m\Omega$  at  $80^\circ C$ . Then the maximum rms voltage across the sense is:

RMS sense voltage =  $15m\Omega \cdot 16A = .24V$

Then  $R_8 = R_9 = .24V / 60\mu A \# 4k\Omega$

Critical current amplifier gain occurs when the current error amplifier slope exceeds the oscillator slope. This condition occurs when:

$V_{oca} f_s = (V_o / L_b) R_{sense} G_{ca}$

$G_{ca}$  = current amplifier gain

$V_{oca}$  = current amplifier output voltage

$f_s$  = switching frequency

$L_b$  = boost inductor value

Then  $G_{ca} = V_{oca} f_s L_b / (V_o R_{sense})$

$= 5 \cdot 45E+3 \cdot 0.8E-3 / 400 \cdot 0.015$

$= 28$

Setting  $G_{ca} \# 25$  enables the calculation of  $R_z$  and  $C_z$ :

$R_z \# G_{ca} R_9 \# 100k\Omega$

$C_z = 1 / 2\pi f_c R_z$  with a crossover frequency  $f_c$  of 10kHz.

then  $C_z = 150pF$ .

Capacitor  $C_p$  can eventually be added to reduce the phase lag of the amplifier.

### IMPLEMENTATION AND SWITCHING BEHAVIOR

Using a double-sided PCB significantly reduces the parasitic inductances of the circuit:

- parasitic inductance  $L_{p1}$  and  $L_{p2}$  shown in figure 1 are intrinsic characteristics of the ISOTOP module itself; these values are very low (less than 10nH).
- parasitic inductances  $L_{p3}$  and  $L_{p4}$  are due to the ISOTOP/capacitor loop. The proposed layout results in about 20 nH for  $L_{p3} + L_{p4}$ .

These values mean that the total voltage overshoot during the turn off of the MOSFET is limited to about 30V with a  $di/dt$  of 1000A/sec with no snubber.

- parasitic inductance  $L_{p5}$  is a few nH due to the use of an active current sense in a TO-218 package. This results in an excellent signal/noise ratio at the current error amplifier input.

The following measurements have been made with the iron powder inductor as described in paragraph 4.

**Figure 5** shows the most important signals with an input voltage of 208Vac and an output power of 1600W. To show the current ripple more clearly, one second persistence has been used. The slight overshoot of the current error amplifier output during the mains zero voltage crossing is due to the rise of the inductor permeability at low induction. Indeed, the inductor size optimisation requires operation with 50% saturation of the iron at maximum peak current.

**Figure 6** shows average values of the waveforms in figure 5.

**Figure 7** shows the input current and voltage with 120Vac mains and 1600W output Power.

**Figure 8** shows the drain voltage and source current during turn off. Note that the source current probing creates a parasitic inductance, limiting the  $di/dt$ . Thus there is no significant turn off over-voltage.

**Figure 9** shows the diode recovery current with a forward current of 20A and a  $di/dt$  of 700A/ $\mu$ sec. Note that the  $R_{gn}$  gate drive resistance can be ad-

## APPLICATION NOTE

justed to tightly control the  $di/dt$ . This is still acting with high  $di/dt$  value due to the low parasitic inductance of the gate drive. Thermal measurements have been performed enabling the junction temperature to be accurately estimated:

with  $V_{in} = 220Vac/I_n = 8Arms$

$$V_{out} = 400Vdc/R_{gn} = 0\Omega$$

MOSFET+DIODE conduction losses = 10W

MOSFET+DIODE commutat. losses = .52W/kHz

with  $V_{in} = 120Vac/I_n = 15Arms$


$$V_{out} = 400Vdc/R_{gn} = 0W$$

MOSFET+DIODE conduction losses = 40W


MOSFET+DIODE commutat. losses = .88W/kHz

with a gate drive resistance  $R_{gn}=102$ , 25% must be added to the commutation losses.


**Figure 5: Current & Voltage Recorders**

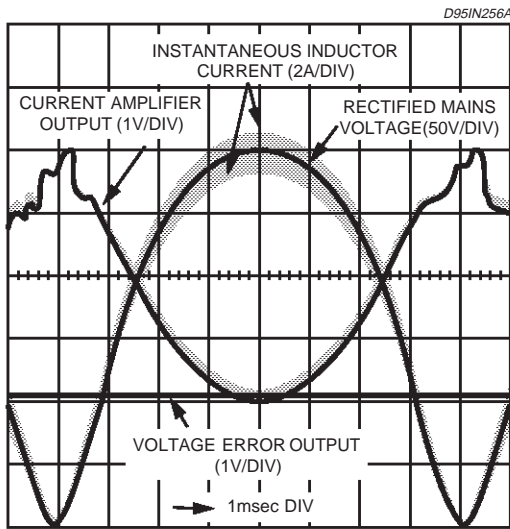


**Figure 6: Average Current & Voltage.**

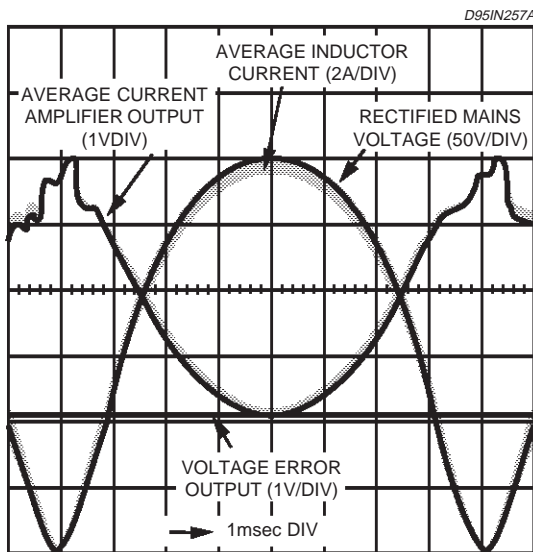


**Figure 7: Average Current & Voltage**

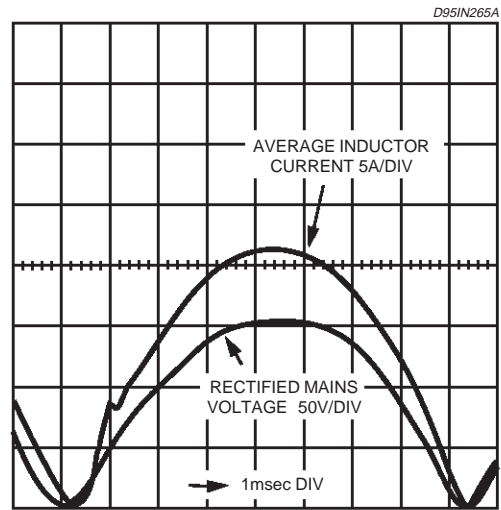

**Figure 8: Turn Off Mosfet Behavior**

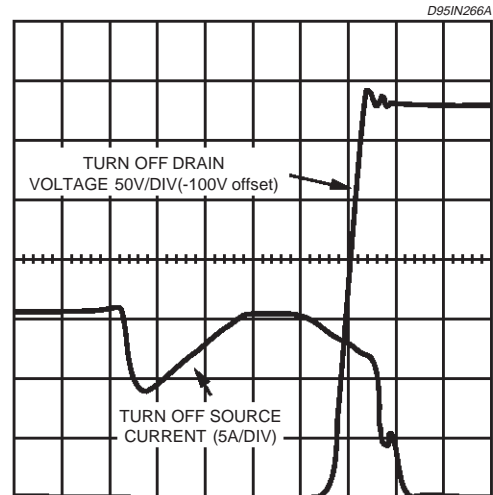

**Figure 9: Diode Recovery Current**

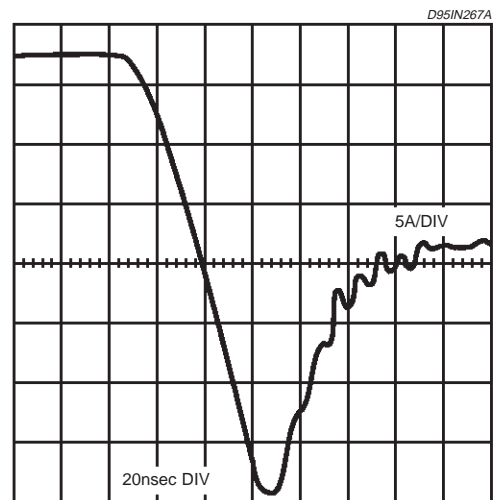

**CONCLUSIONS**

This paper presents an optimized Power Factor Corrector built around a power module driven by the L4981 control IC. This STE36N50-DK ISO-TOP power module is mounted directly on the PCB providing both very low inductance layout and compact hardware.

Eliminating parasitic inductances enables tight control of switching di/dt and prevents turn off overvoltage. Therefore faster switching speeds are allowed to reduce switching losses. The 2Amps current capability of the controller is also a useful feature.

Combined with a single layer winding inductor, such a configuration results in very low EMI and RFI generation.

Finally, there is potential for further improvements using two features of the L4981:

- the possibility either to synchronize the IC with an external signal, or to modulate the PFC switching frequency to spread the RFI noise.
- the extra multiplier input, which enables external compensation.

## APPLICATION NOTE

---

Information furnished is believed to be accurate and reliable. However, SGS-THOMSON Microelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of SGS-THOMSON Microelectronics. Specification mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. SGS-THOMSON Microelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of SGS-THOMSON Microelectronics.

© 1997 SGS-THOMSON Microelectronics – Printed in Italy – All Rights Reserved

SGS-THOMSON Microelectronics GROUP OF COMPANIES

Australia - Brazil - Canada - China - France - Germany - Italy - Japan - Korea - Malaysia - Malta - Morocco - The Netherlands -  
Singapore - Spain - Sweden - Switzerland - Taiwan - Thailand - United Kingdom - U.S.A.



LittleDiode supplies new, hard to find or obsolete electronic components and semiconductors all over the world.

With over two million different components listed you are sure to find the part you need.

Feel free to visit us today at our online store:

[LittleDiode.com](http://LittleDiode.com)

Looking forward to providing you with the best possible service.