

## 1500W - 440V POWER FACTOR CORRECTOR PREREGULATOR

The application here described has been tailored to supply a three phase inverter for motion control (see fig.1). To reduce the current in the switches of the inverter, the output voltage of the power factor has been held quite high.

The target specification of the PFC application is:

Mains supply  $V_{in}(rms)$  = 220Vac  $\pm$ 20%  
 (f = 50/60Hz)

Output Voltage  $V_{out}$  = 440Vdc

Output Power  $P_{out}$  = 1500W

A switching frequency of 60kHz has been chosen as a good compromise between requirements of small size magnetics and low switching losses.

For this application a full isolated ISOTOP(TM) STE30NA50-DK has been used.


This module is especially intended for boost applications and consists off the integration of a low RDS/500V Mosfet with a TURBOSWITCH(TM) diode.

The use of the module allows a compact and ef-

fective solution in terms of layout and power dissipation. The output stage of the L4981A/B is capable of driving directly the module without the aid of a buffer stage. The L4981A controller is supplied by the auxiliary of the boost inductor, a Graetz bridge and a simple resistor for the start-up phase. The Output capacitor filter has been realized connecting in parallel four tap in "series" configuration. This solution allows the use standard parts, in terms of the rated voltage, resulting easier to be implemented in comparison with a "single" configuration. To be noted that the high frequency filter (C1 + C2) has been split in two parts. In this way it is possible to held a low value capacitor (C2) connected to the output of the rectifier bridge, minimising the harmonic distortion (introduced by the rectified DC contents). On the other hand, the capacitor (C1) connected to the AC side of the bridge, performs most of the high frequency filter function without introducing DC content.

The schematic circuit is shown in fig.1

Figure 1: Schematic Diagram

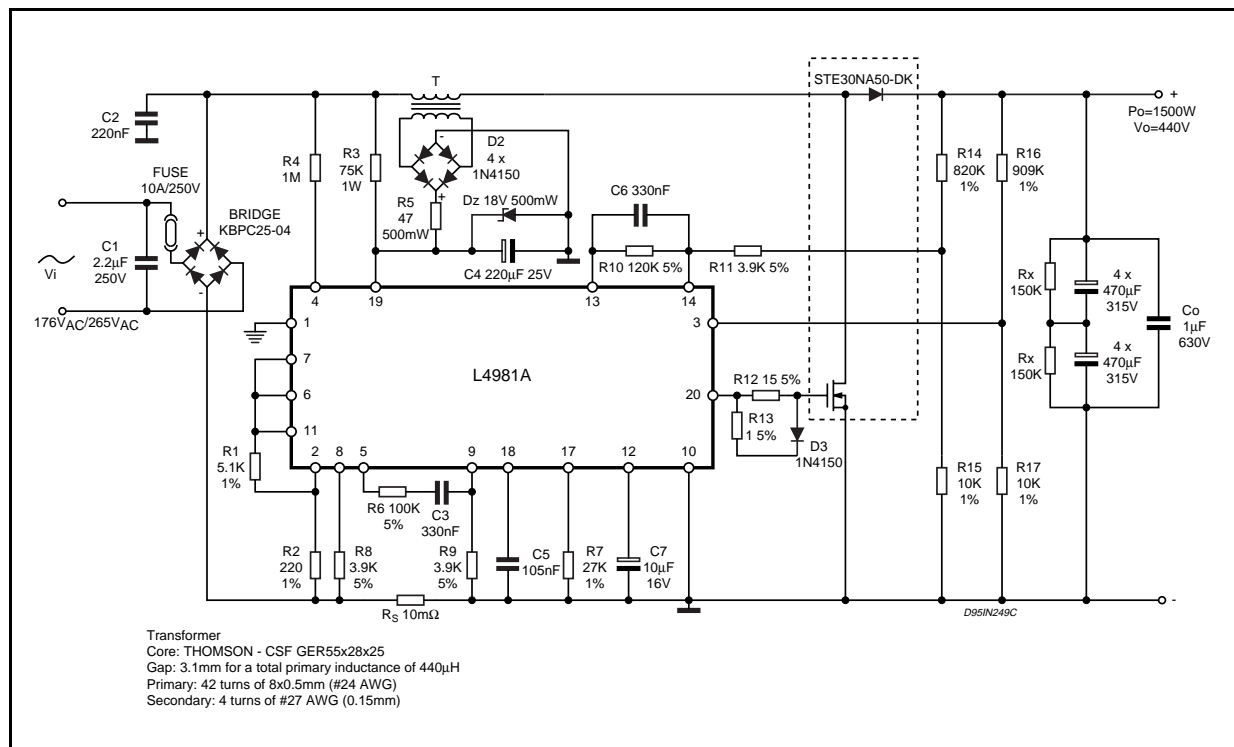

## APPLICATION NOTE

### L4981A PARTS LIST

<p>Boost inductor (T) L = 0.44mH          Core :Thomson - E 55x28x25          Gap = 3mm          Primary Turns = 42 (8 x 0.5mm)          Secondary Turns = 4 (0.15mm)</p> <p>Co= 940<math>\mu</math>F = [(4 + 4) x 470<math>\mu</math>F/315V + 1<math>\mu</math>F/630V]          C1 = 2.2<math>\mu</math>F/250Vac          C2 = 220nF/630V          C3 = 330nF          C4 = 220<math>\mu</math>F/25V          C5 = 1.5nF          C6 = 330nF          C7 = 10<math>\mu</math>F</p> <p>Power Switch = STE30NA50-DK          Input Bridge = KPBC25-04</p> <p>D2 = 1N4150 (X 4)          D3 = 1N4150</p>	<p>Rs = 10m<math>\Omega</math> /1W          R1 = 5.1k<math>\Omega</math> /1%          R2 = 220<math>\Omega</math> /1%          R3 = 75k<math>\Omega</math>/1<math>\Omega</math>          R4 = 1M          R5 = 47 /1/2<math>\Omega</math>          R6 = 100k<math>\Omega</math>          R7 = 27k /1%          R8 + R9 = 3.9k<math>\Omega</math>          R10 = 120k<math>\Omega</math>          R11 = 3.9k<math>\Omega</math>          R12 + R13 = 15<math>\Omega</math>          R14 = 820k<math>\Omega</math> /1%          R15 = 10k<math>\Omega</math> /1%          R16 = 909k<math>\Omega</math>          R17 = 10k<math>\Omega</math></p>
--	---

**Table 1:** Test Result.

Mains rms (V)	Vout (V)	Pout (W)	Power Factor	Harmonic Distortion (%)		Efficiency (%)
				THD	AH3	
176	451	509	0.998	2.0	1.9	94.2
176	444	937	0.999	1.4	1.3	94.0
176	438	1396	0.999	1.0	0.9	94.0
220	451	509	0.996	2.1	1.9	95.6
220	445	941	0.998	1.5	1.4	95.2
220	438	1396	0.999	1.0	0.9	95.3
260	452	511	0.993	2.5	1.9	95.1
260	446	945	0.997	1.4	1.3	96.4
260	439	1402	0.999	1.1	0.8	96.1

### CONCLUSIONS

The evaluation has been done using the "A" version of the L4981 controller, without using additional features obtaining high performance results, in terms of efficiency and harmonic content.

Further improvements are possible using the additional features of the I.C. such as the LFF (pin 16) for the best control of the output voltage or by the use of the B version to minimise the EMI filter.

Information furnished is believed to be accurate and reliable. However, SGS-THOMSON Microelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of SGS-THOMSON Microelectronics. Specification mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. SGS-THOMSON Microelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of SGS-THOMSON Microelectronics.

© 1997 SGS-THOMSON Microelectronics – Printed in Italy – All Rights Reserved

SGS-THOMSON Microelectronics GROUP OF COMPANIES

Australia - Brazil - Canada - China - France - Germany - Italy - Japan - Korea - Malaysia - Malta - Morocco - The Netherlands -  
Singapore - Spain - Sweden - Switzerland - Taiwan - Thailand - United Kingdom - U.S.A.



LittleDiode supplies new, hard to find or obsolete electronic components and semiconductors all over the world.

With over two million different components listed you are sure to find the part you need.

Feel free to visit us today at our online store:

[LittleDiode.com](http://LittleDiode.com)

Looking forward to providing you with the best possible service.