


2.3W DUAL AUDIO POWER AMPLIFIER

The KA2206 is a monolithic integrated circuit consisting of a 2-channel power amplifier. It is suitable for stereo and bridge amplifier application of radio cassette tape recorders.

FEATURES

- High output power
Stereo: $P_o = 2.3W$ (Typ) at $V_{cc} = 9V$, $R_L = 4\Omega$.
Bridge: $P_o = 4.7W$ (Typ) at $V_{cc} = 9V$, $R_L = 8\Omega$.
- Low switching distortion at high frequency.
- Small shock noise at the time of power on/off due to a built-in muting circuit
- Good ripple rejection due to a built-in ripple filter.
- Good channel separation.
- Soft tone at the time of output saturation.
- Closed loop voltage gain fixed 45dB (Bridge: 51dB) but availability with external resistor added.
- Minimum number of external parts required.
- Easy to design radiator fin.

12 DIP/F

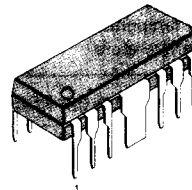

ORDERING INFORMATION

Device	Package	Operating Temperature
KA2206	12 DIP/F	-20°C ~ 70°C

BLOCK DIAGRAM

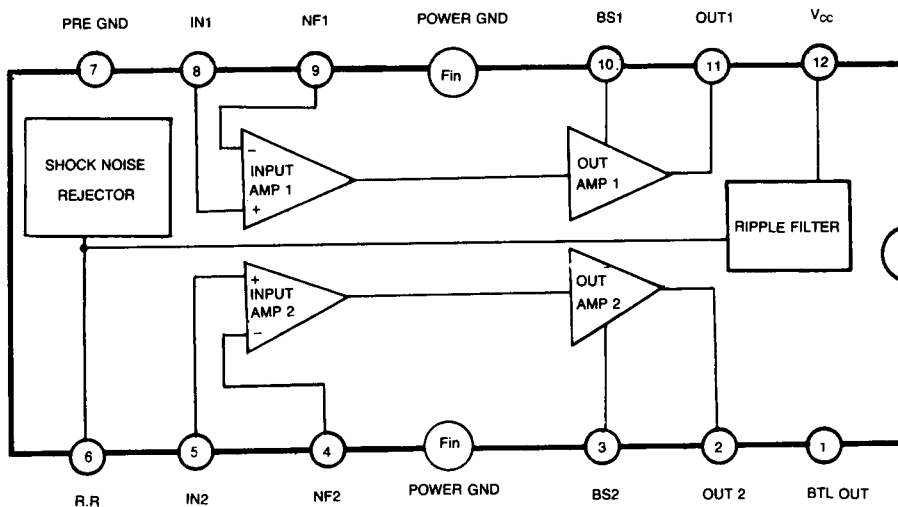


Fig. 1

ABSOLUTE MAXIMUM RATINGS ($T_a=25^\circ\text{C}$)

Characteristic	Symbol	Value	Unit
Supply Voltage	V_{CC}	15	V
Power Dissipation	P_D	4*	W
Operating Temperature	T_{OPR}	-20 ~ +70	$^\circ\text{C}$
Storage Temperature	T_{STG}	-40 ~ +150	$^\circ\text{C}$

* Fin is soldering on the PCB


ELECTRICAL CHARACTERISTICS

($T_a=25^\circ\text{C}$, $V_{CC}=9\text{V}$, $f=1\text{KHz}$ $R_G=600\Omega$, unless otherwise specified)

Characteristic	Symbol	Test Conditions	Min	Typ	Max	Unit	
Operating Supply Voltage	V_{CC}			9	11	V	
Quiescent Circuit Current	I_{CCQ}	$V_i=0$, Stereo		40	55	mA	
Closed Loop Voltage Gain	G_{VC}	Stereo	$V_i=-45\text{dBm}$	43	45	47	dB
		Bridge		49	51	53	dB
Channel Balance	CB	Stereo	-1	0	+1	dB	
Output Power	P_O	Stereo	$R_L=4\Omega$, THD=10%	1.7	2.3		W
			$R_L=8\Omega$, THD=10%		1.3		W
		Bridge	$R_L=8\Omega$, THD=10%		4.7		W
Total Harmonic Distortion	THD	Stereo	$P_O=250\text{mW}$, $R_L=4\Omega$		0.3	1.5	%
		Bridge				0.5	
Input Resistance	R_i		21	30		K Ω	
Ripple Rejection Ratio	RR	Stereo, $R_G=0\Omega$, $V_i=150\text{mV}$ $f=100\text{Hz}$	40	46		dB	
Output Noise Voltage	V_{NO}	Stereo, $R_G=0\Omega$		0.3	1.0	mV	
		Stereo, $R_G=10\text{K}\Omega$		0.5	2.0	mV	
Cross Talk	CT	Stereo, $R_G=10\text{K}\Omega$, $V_o=0\text{dBm}$	40	55		dB	

APPLICATION INFORMATION

1. Stereo application

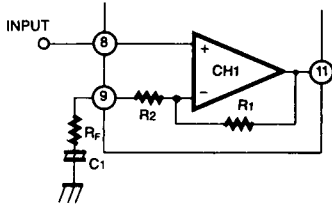


i) Fixed voltage gain
(Pin 9 connected to GND directly)

$$G_v = 20 \log \frac{R_1}{R_2} \text{ (dB)}$$

ii) Variable voltage gain
(Rf and C1 connected with pin 9)

$$G_v = 20 \log \frac{R_1}{R_2 + R_f} \text{ (dB)}$$

2. Bridge application

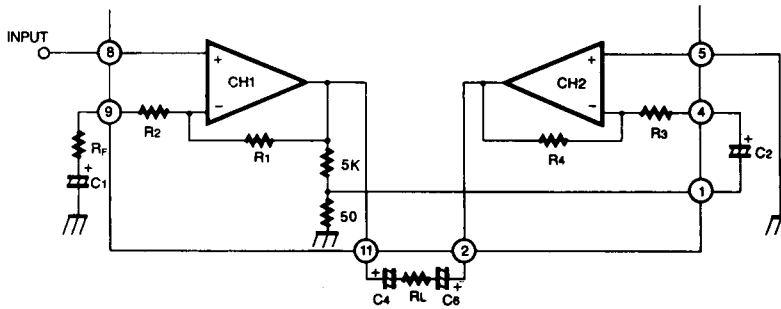

i) Fixed voltage gain (Pin 9 connected to GND directly)

$$G_v = 20 \log \frac{R_1}{R_2} + 6 \text{ (dB)}$$

ii) Variable voltage gain Rf and C1, connected with pin 9)

$$G_v = 20 \log \frac{R_1}{R_2 + R_f} + 6 \text{ (dB)}$$

APPLICATION CIRCUIT

1. Stereo Amplifier

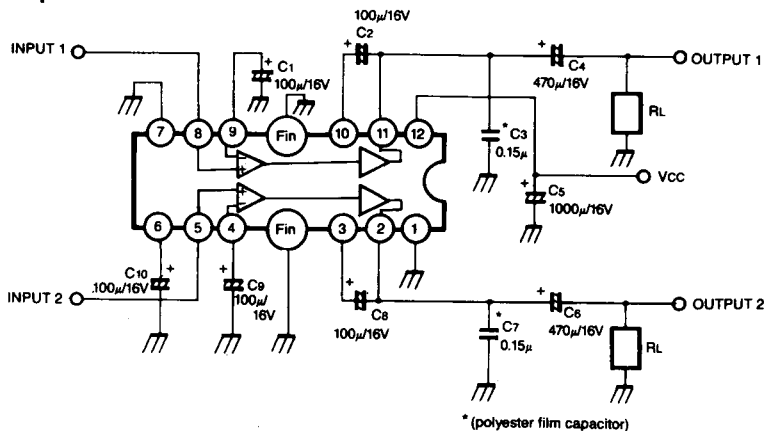


Fig. 2

2. Bridge Amplifier

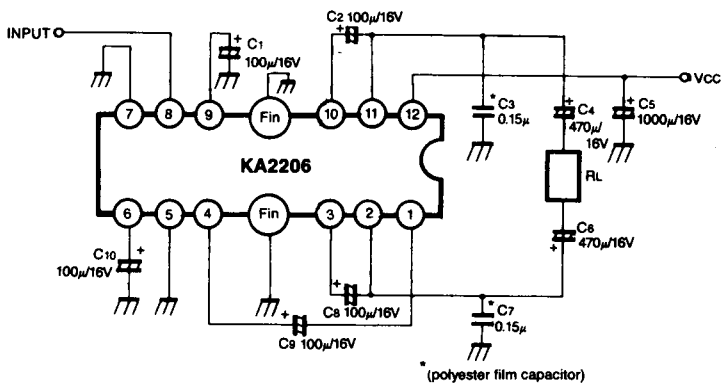


Fig. 3



LittleDiode supplies new, hard to find or obsolete electronic components and semiconductors all over the world.

With over two million different components listed you are sure to find the part you need.

Feel free to visit us today at our online store:

LittleDiode.com

Looking forward to providing you with the best possible service.